

LAB 1

❖ Design Following Circuits using Data Flow Modeling

1. Multiplexer 4x1
2. Demultiplexer 1x4
3. Encoder 8x3
4. Decoder 3x8
5. Half Adder
6. Full Adder
7. 4-bit Full Adder
8. BCD to 7 Segment Display