

Lab 2

1. Design Decoders with following specifications
 - a. 2:4 using gate level modeling.
 - b. 4:16 using shift operator.
2. Design 8:3 priority encoder using dataflow modeling.
3. Design configurable full adder using parameter construct (Test it for 8 bit and 16 bit full adder). Use \$Strobe for Displaying result on transcript.
4. Implement $Y = A|B|C + A.B.E + |B.C + C|D$ using delay value 3 for and gates, 2 for or gates and 4 for not gates. Use two inputs and, or gates only. Use \$Monitor for displaying result on transcript ,also turn off display for 50 time units and then continue displaying the results.
Note: $|B|C$ means (not B) and (not c)
5. Design parallel in parallel out 8-bit rotational right shift register with a clock, synchronous load input using
 - a. Blocking
 - b. Non-Blocking.
6. Design 16:1 mux using case statements.
7. Design 8:3 priority encoder using casez statements.
8. Design the following circuits
 - a. D latch with reset using if-else statement.
 - b. D flip-flop using latch designed above. Verify whether flip-flop has synchronous or asynchronous reset.
 - c. D flip-flop with asynchronous reset using If-else Statement.