

Lab 7

1. Study datasheet of Asynchronous RAM (CY6264). Also Design and verify the functionality of this RAM.
2. Using switch level modeling (MOS Switches), Design the following:
 - a. 3 input NAND gate
 - b. 3 input NOR gate
 - c. 2 input XOR gate
3. Design a 4x4 sequential multiplier using booth's algorithm